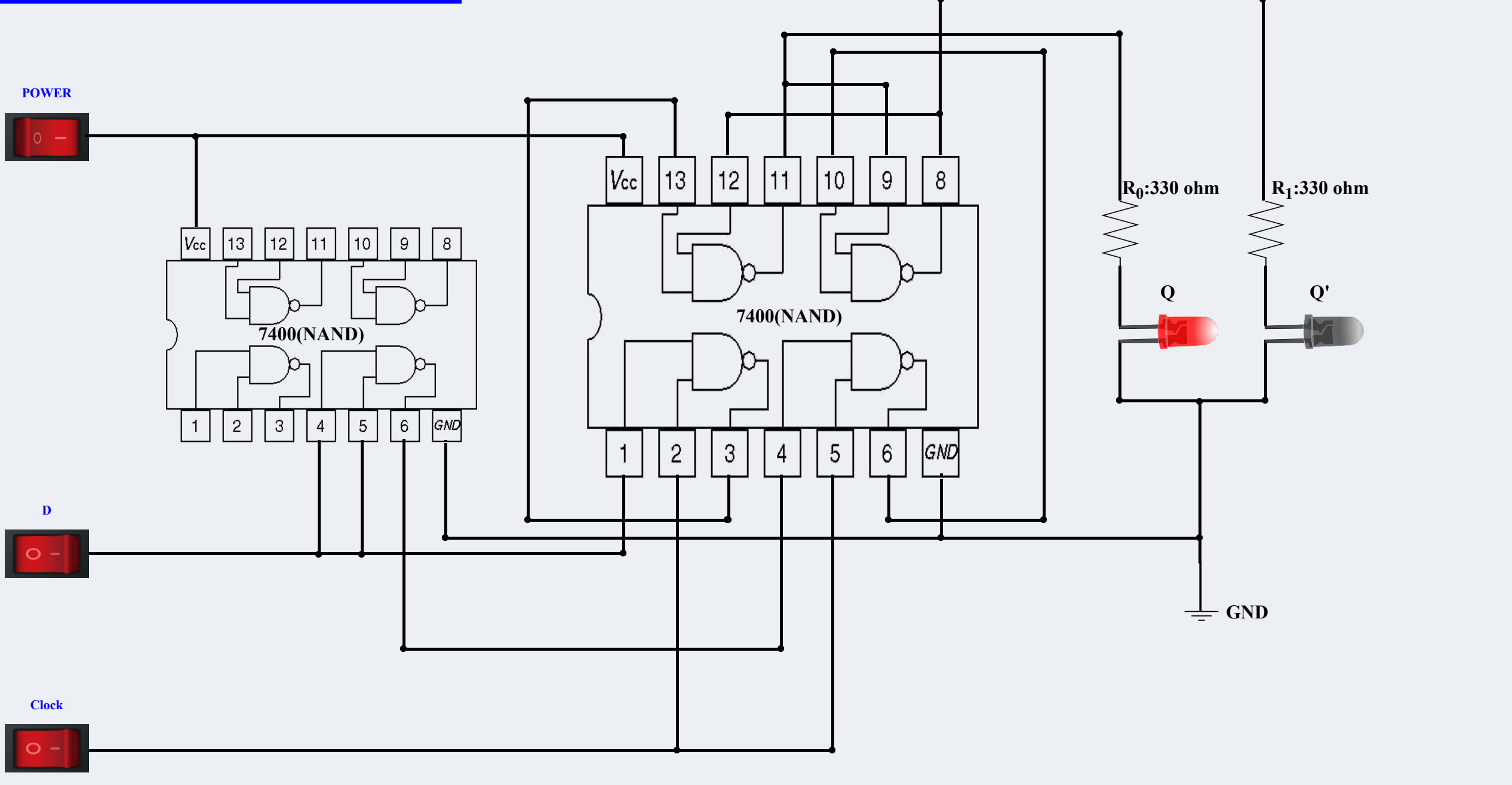


INSTRUCTIONS

Experiment to perform logic of D - Flipflop on kit



TRUTH TABLE								PRINT	Add
Serial No.	clock	D	Q(n-1)	Q'(n-1)	Q	Q'	Remark		
1	0	0	X	X	0	1	No Change		
2	1	0	0	1	0	1	Reset		
3	0	1	0	1	0	1	No change		
4	1	1	0	1	1	0	set		

