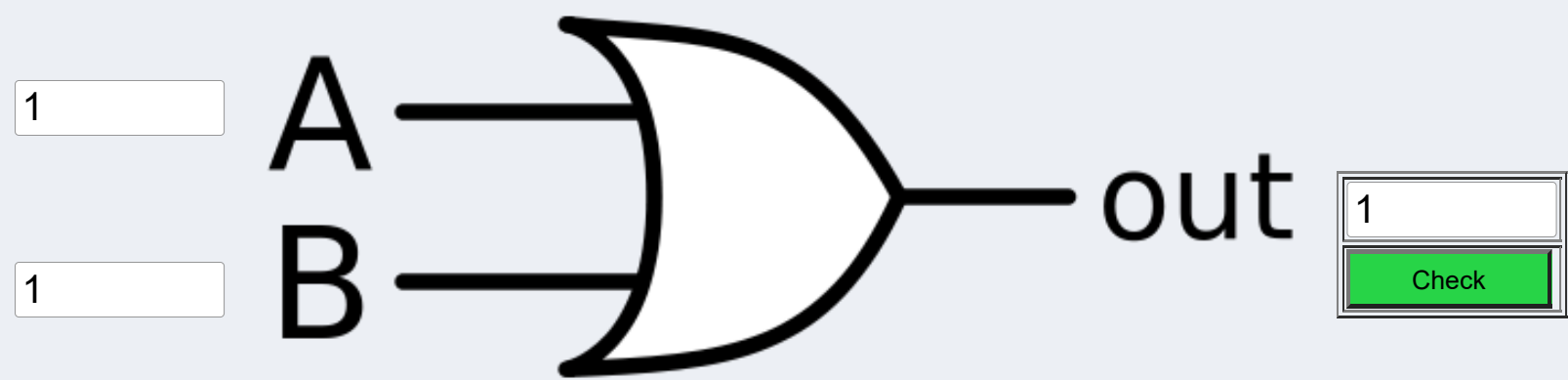


INSTRUCTIONS

Verification of truth table for OR gate



TRUTH TABLE					Print
Serial No.	A	B	Output	Remarks	
1	0	0	0	Correct	
2	0	1	1	Correct	
3	1	0	1	Correct	
4	1	1	1	Correct	

Reset