INSTRUCTIONS

Experiment to perform logic of Ex-NOR Using Nand on left

Y=(A.(AB))*.(B.(AB)*)

Y=(A.(AB))*.(B.(AB)*)

Y=(A.(AB))*.(B.(AB)*)

Oneck Reset PRINT Nied

https://de-iitr.vlabs.ac.in/exp/realization-of-logic-functions/simulation/images/All gates/nand4.html

Ex-NOR using Nand gate