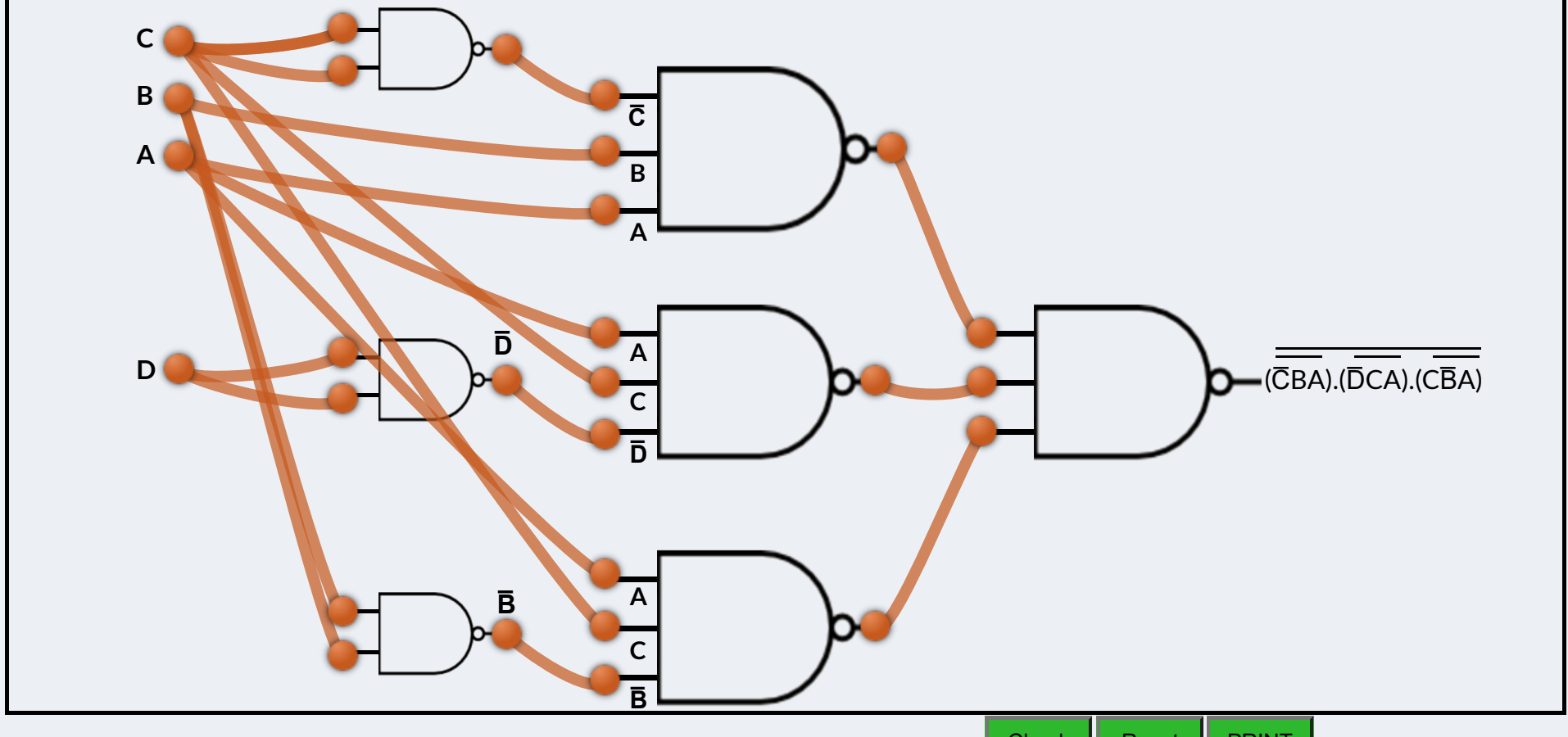


INSTRUCTIONS

Experiment to perform logic of Expression Using Nand on kit

$F = (CBA), (B\overline{C}A), (C\overline{B}A)$



Check

Reset

PRINT