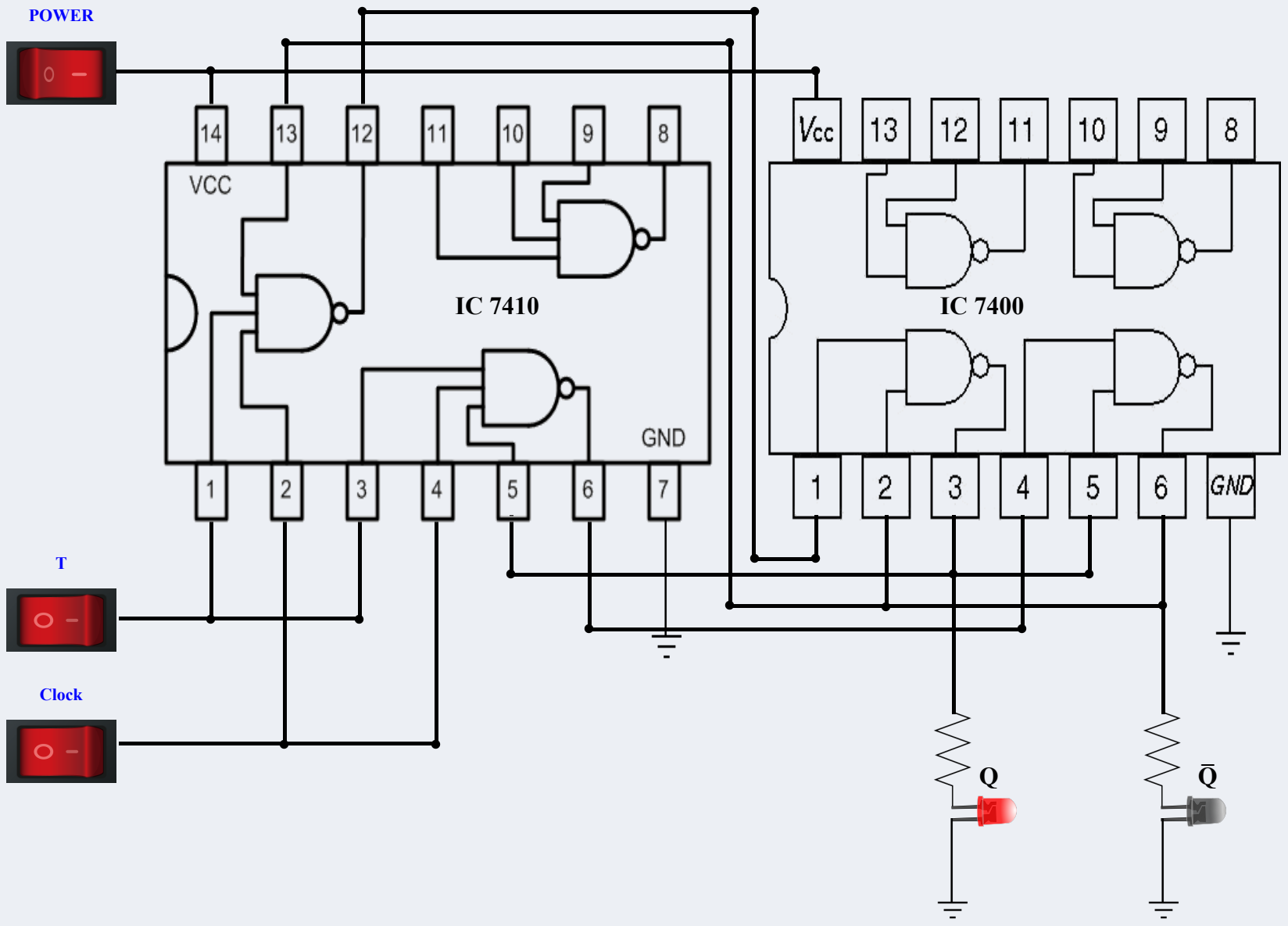


INSTRUCTIONS

Experiment to perform T Flip Flop on kit



TRUTH TABLE							Add	Print
Serial No.	Clock	T	Q _{n-1}	Q _{n-1}	Q	Q	Remarks	
1	0	0	X	X	0	1	No Change	
2	1	0	0	1	0	1	No change	
3	0	1	0	1	0	1	No Change	
4	1	1	0	1	1	0	Toggle	

