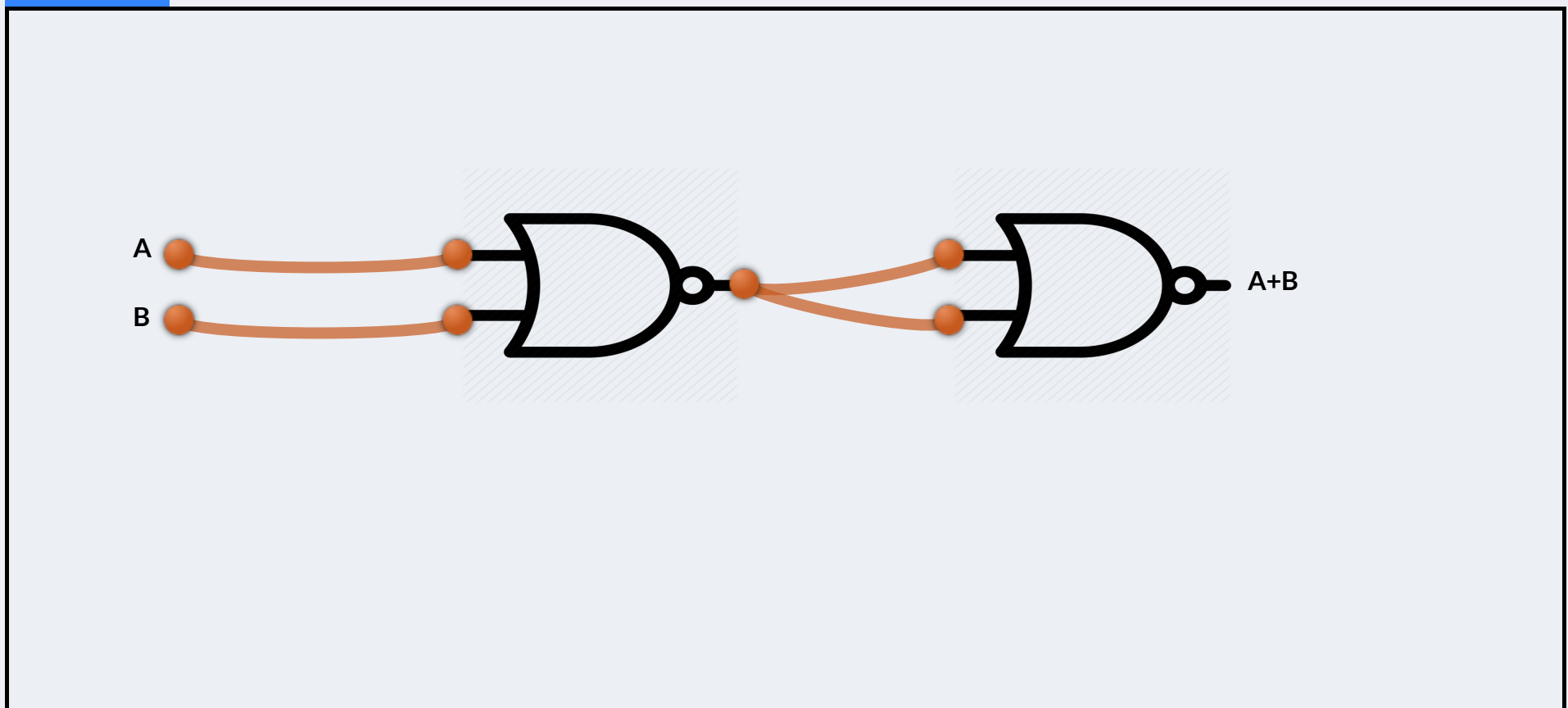


INSTRUCTIONS

Experiment to perform logic of OR Using NOR on kit

Y=A+B



Check Reset PRINT Next