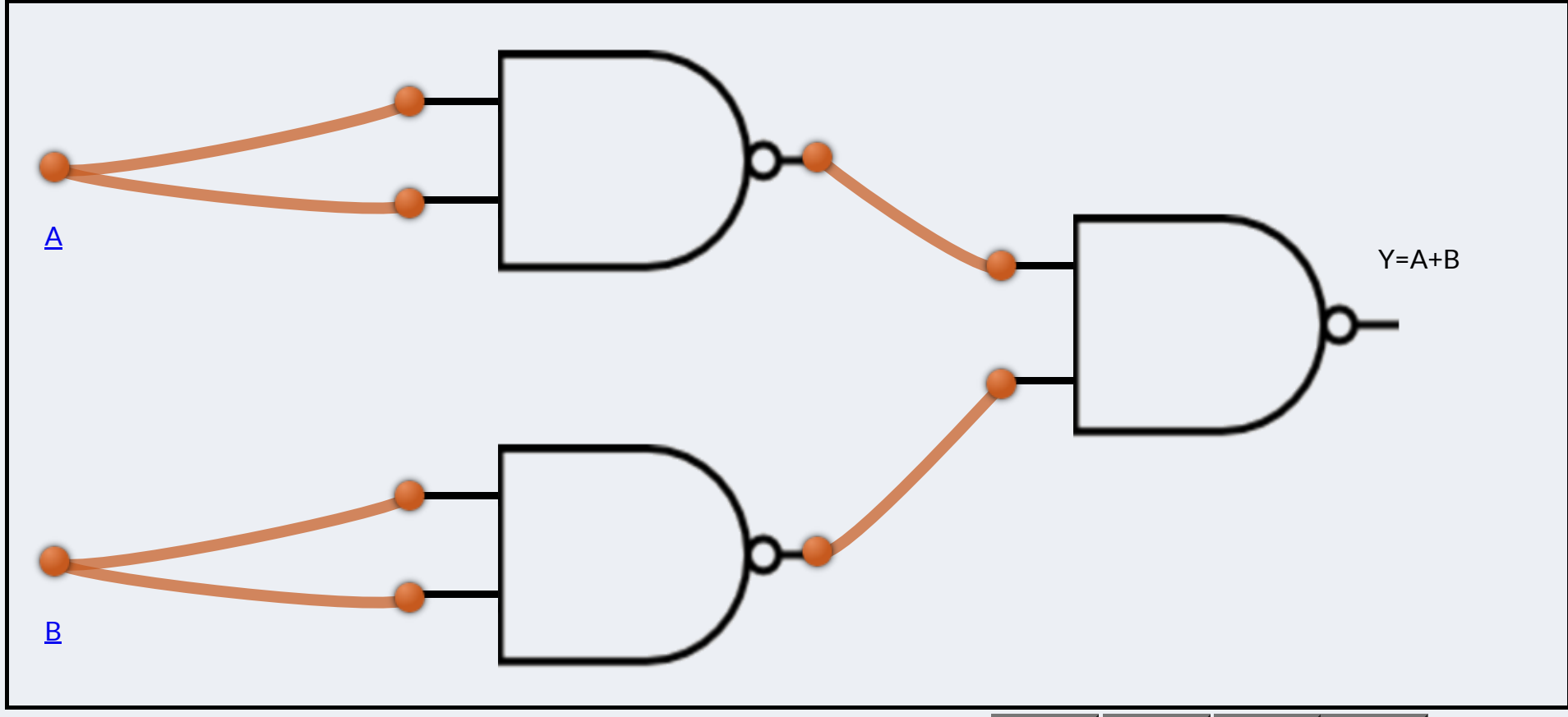


INSTRUCTIONS

Experiment to perform logic of Or Using Nand on kit

Y=A+B



Check Reset PRINT Next