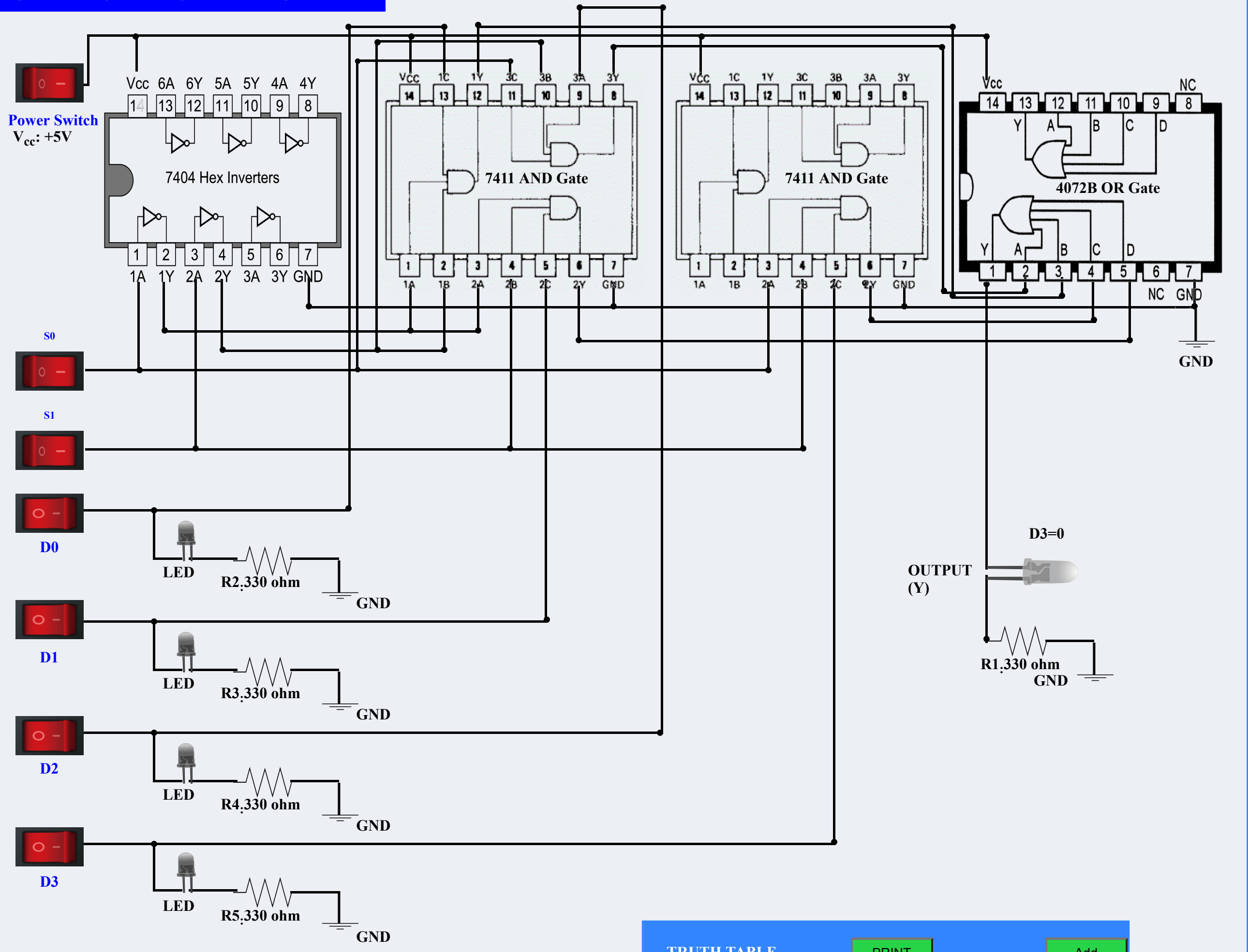


INSTRUCTIONS

Experiment to perform logic of 4:1 Multiplexer on kit



TRUTH TABLE				PRINT	Add
Serial No.	S0	S1	OUTPUT (Y)	OUTPUT VALUE	
1	0	0	D0	0	
2	0	1	D1	0	
3	1	0	D2	0	
4	1	1	D3	0	