

INSTRUCTIONS

Experiment to perform logic of Ex-OR using NOR on kit

