

INSTRUCTIONS

Experiment to perform logic of And Using Nor on kit

