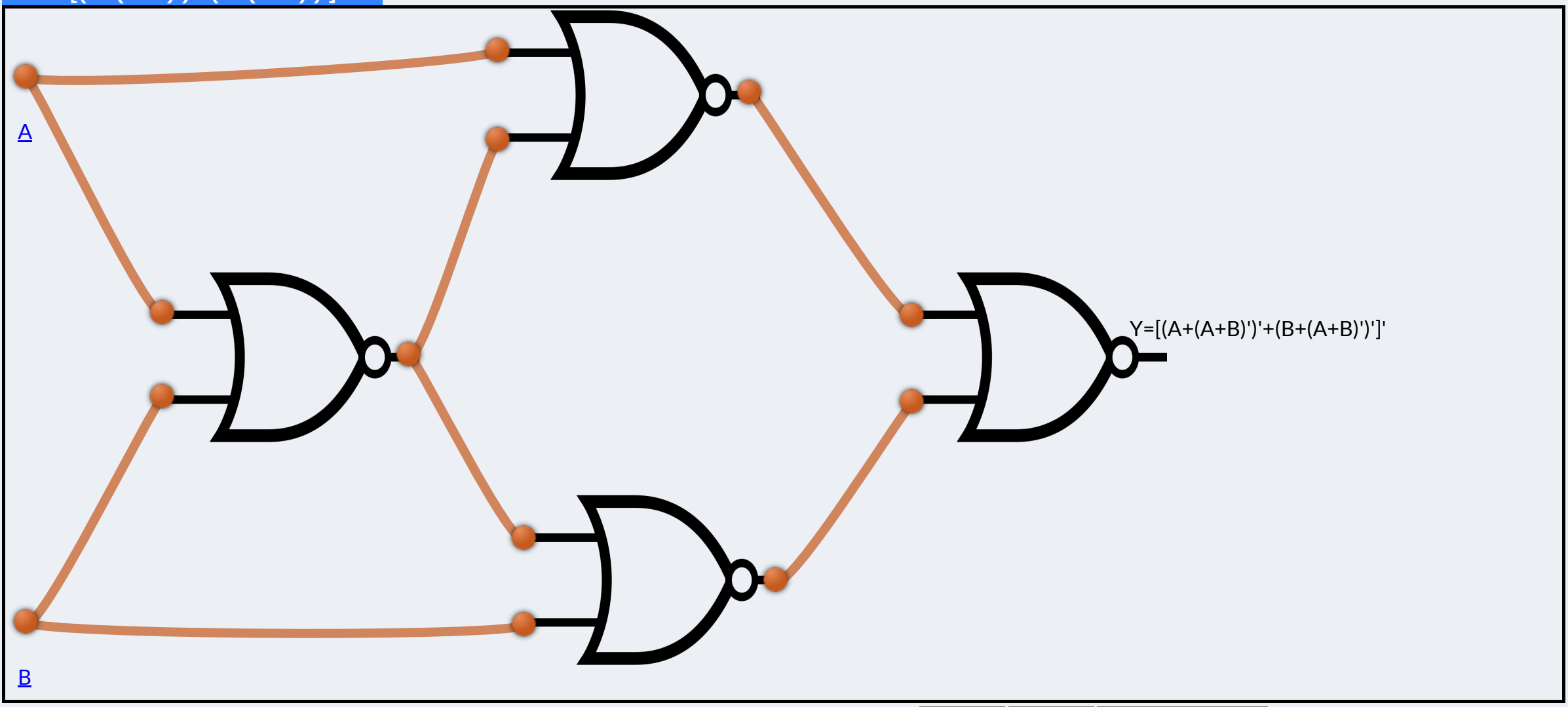


INSTRUCTIONS

Experiment to perform logic of Ex-NOR Using Nor on kit

$$Y = [(A + (A + B))' + (B + (A + B))']'$$



Check Reset PRINT Next