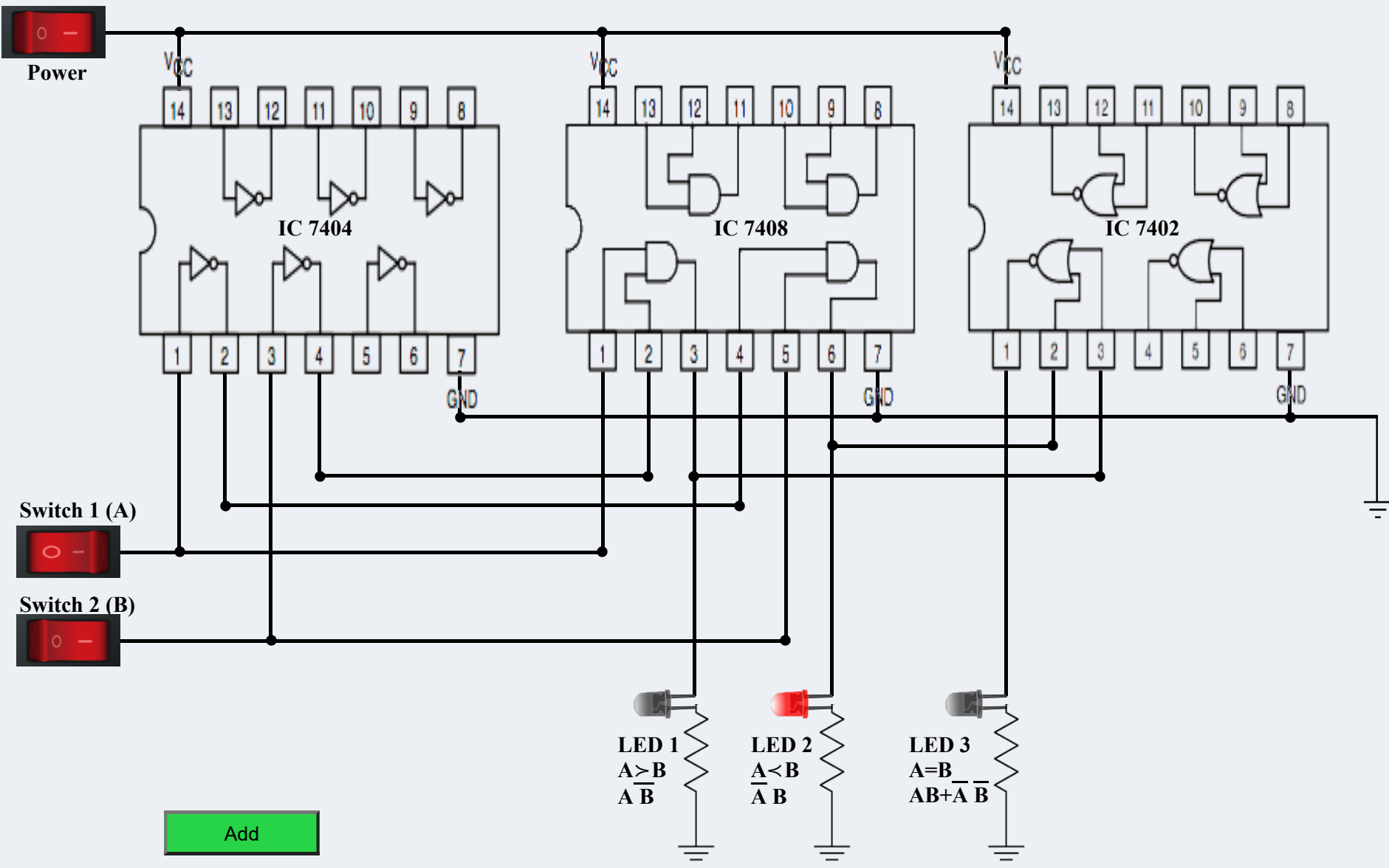


Instructions

Construction of 1-Bit Comparator and verification of its operation

Print



Add

TRUTH TABLE

Serial No.	A	B	A>B	A<B	A=B
1	0	0	0	0	1
2	1	0	1	0	0
3	1	1	0	0	1
4	0	1	0	1	0